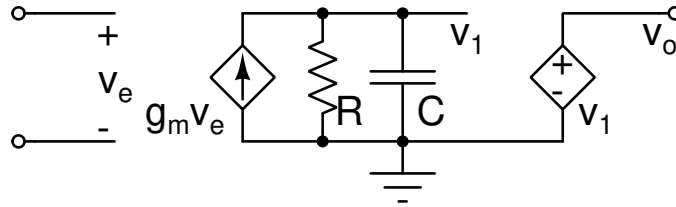


**Mini-project 2**

1. Find DC gain and UGB of the opamp LT1013 using LTspice. Use this information to determine the component values of following LT1013 linear macro-model:

**Figure 1:** Opamp macro-model

Include the following in report:

- Screenshot of test-bench to find gain and UGB.
  - Macro-model with its component values.
  - Frequency response of LT1013 and its macro-model in the same plot with clear annotations of important points. (Use AC analysis)
  - Comments.
2. Design an instrumentation amplifier using LT1013 including biasing and coupling to realize this operation:

$$V_o = 4(V_1 - V_2)$$

Specifications:

- $V_1$  and  $V_2$  frequency range: 1 kHz-10 kHz
- Less than 0.1 dB gain variation in signal frequency
- Load: 10 k $\Omega$ . Signal source: Ideal voltage source. Both load and source are single-ended.
- Supply: Single 30 V source
- Total bias current excluding opamp: <1 mA
- Use resistor values between 1 k $\Omega$  - 100 k $\Omega$

Objective is to meet the specs while using minimum value for capacitors and maximizing CMRR.

Include the following in report:

- Screenshot of LTspice schematic with component values.
- Frequency response plots w.r.t. one input at a time overlaid in the same window. (AC analysis)
- Output magnitude plot when both the inputs have AC magnitude equal to 1. (AC analysis)
- Comments.